
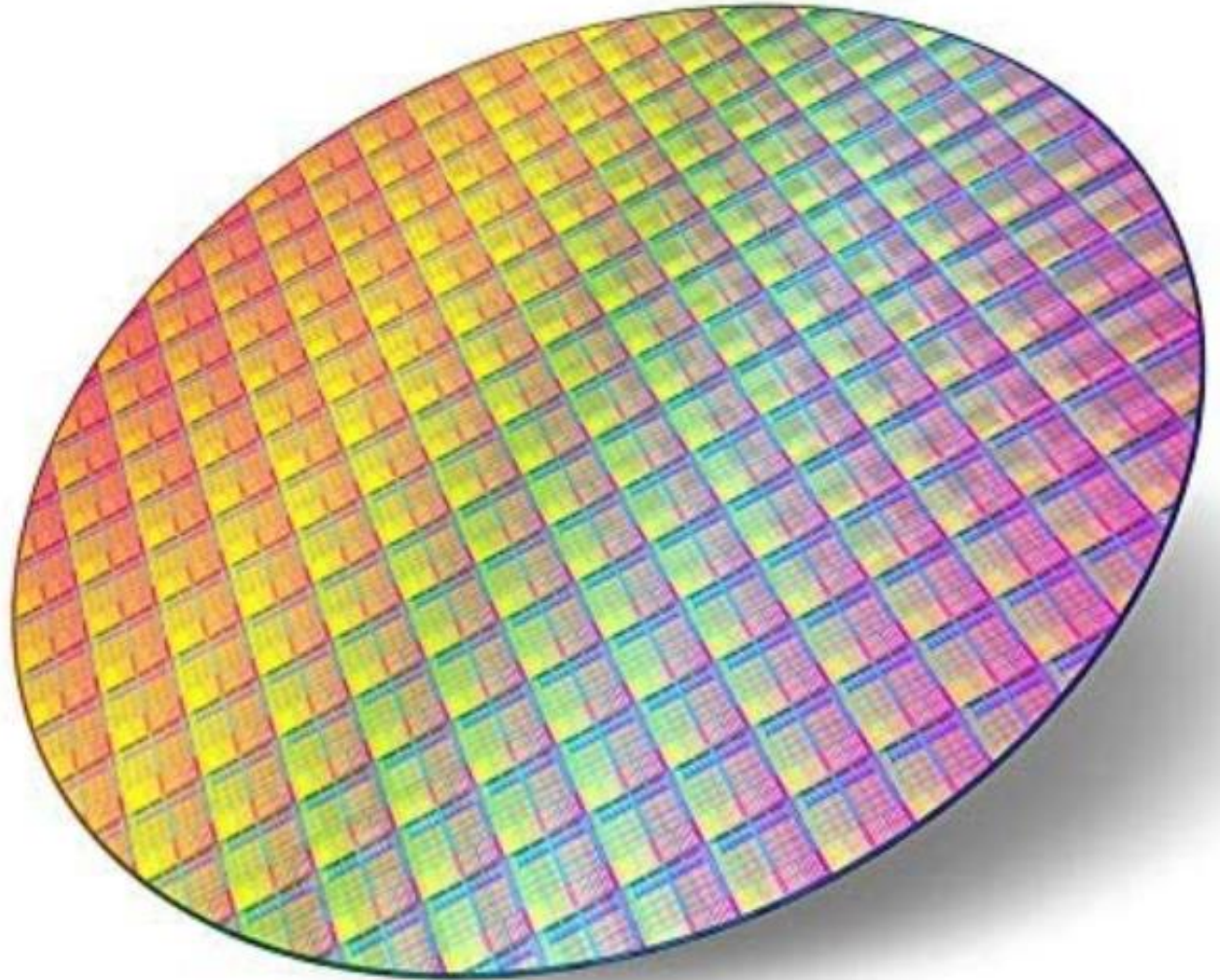


Chip Day,


DTU,
April 2022

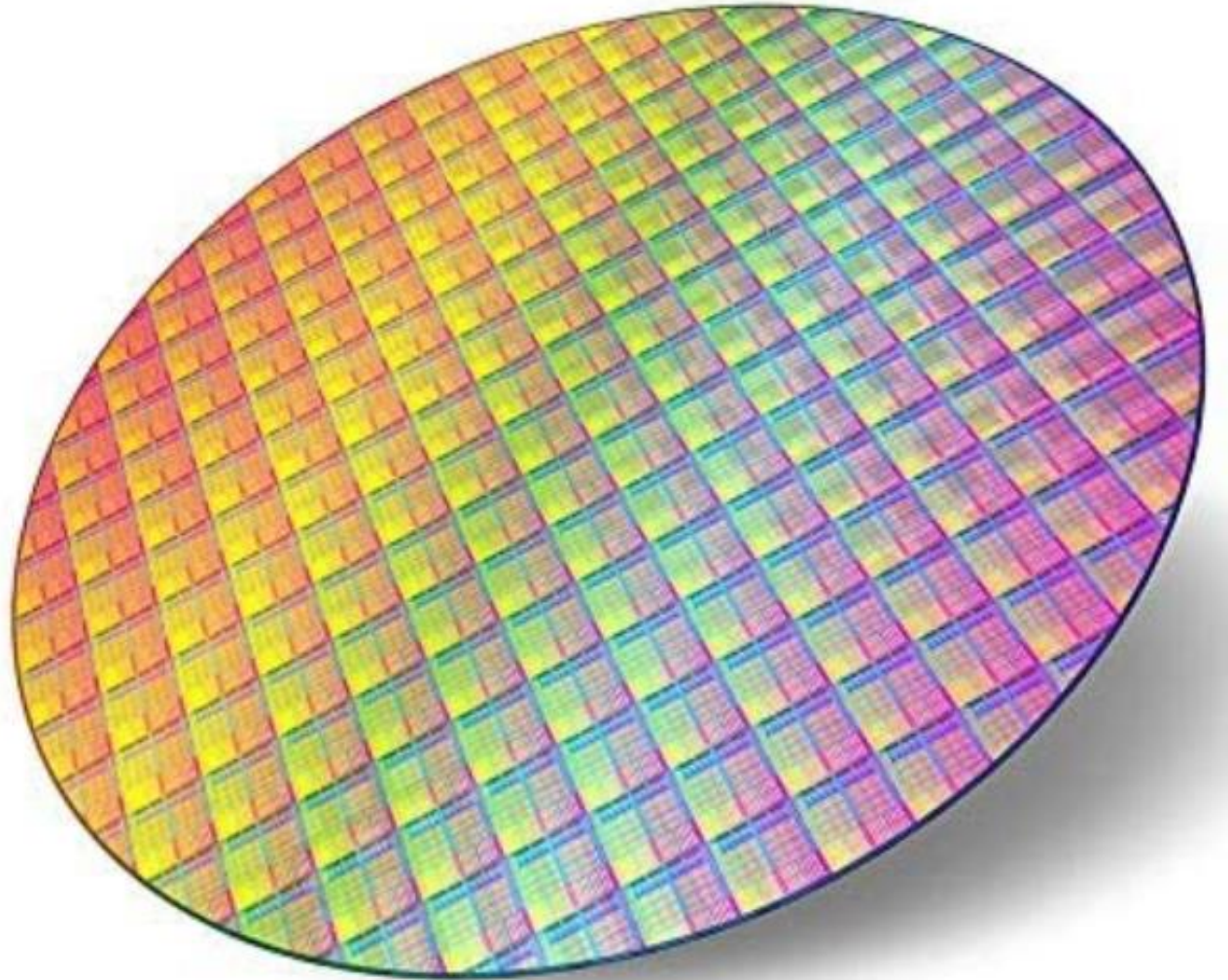

Analog IC design



Who are we?

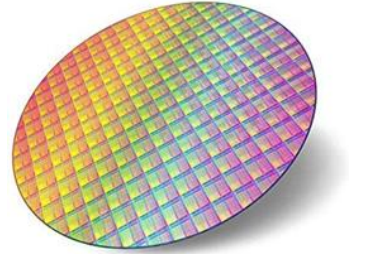

Calvin Maxsen de Oliveira
Analog IC Designer at Oticon

oticon



Jakob Graversgaard Thomsen
Analog IC Designer at Oticon

oticon




Pere Llimós Muntal
CEO at Skycore Semiconductors

Skycore[®]
Semiconductors




Agenda – Analog IC design

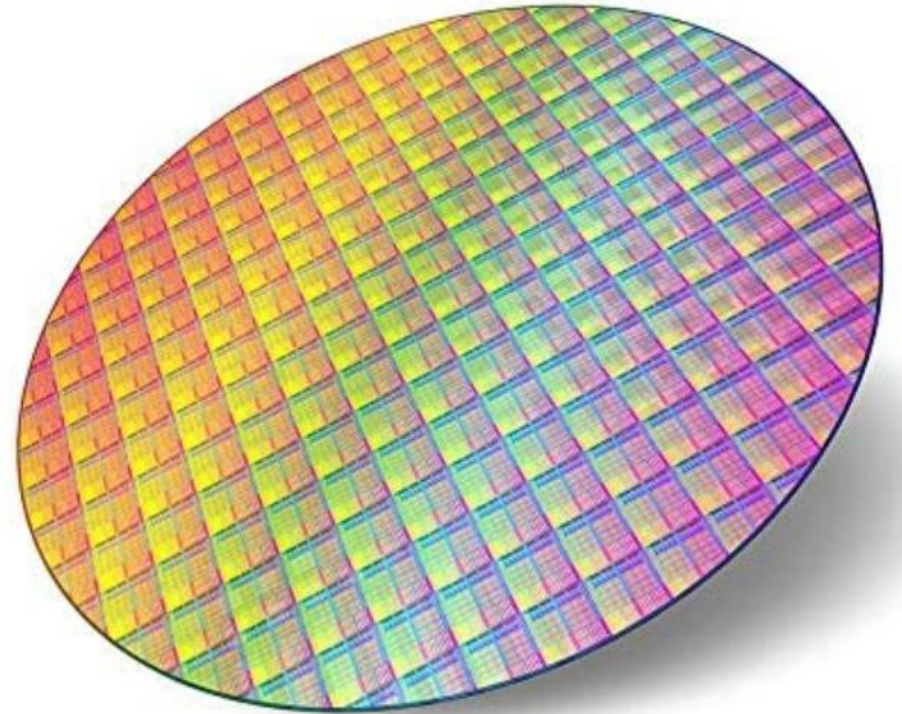- Background: What is Analog IC Design?
- Analog IC design in Audio Systems
- Analog IC design in Power Conversion






Agenda – Analog IC design



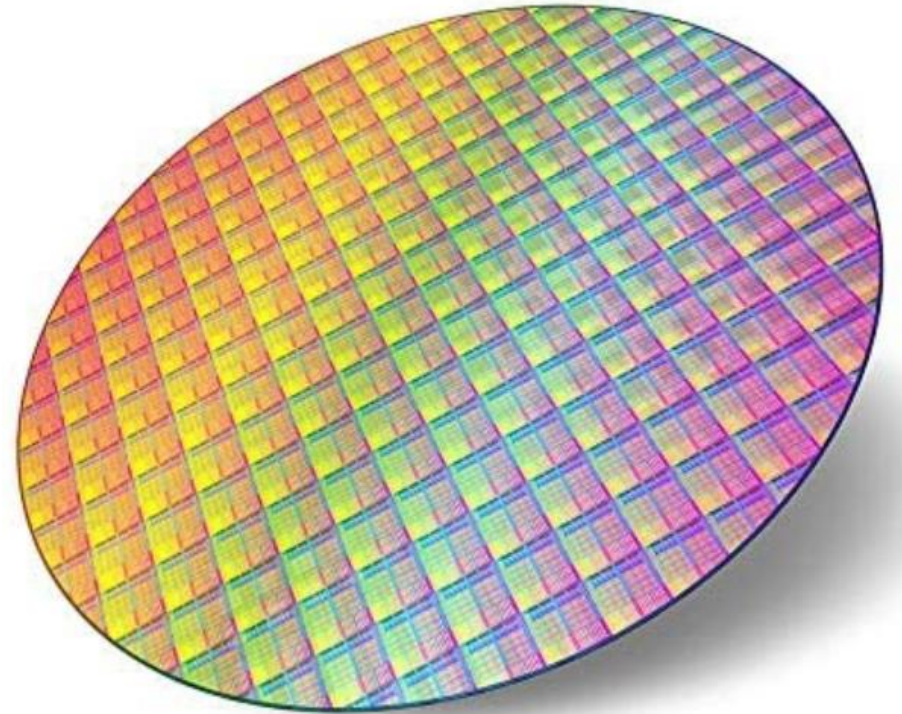
- Background: What is Analog IC Design?
- Analog IC design in Audio Systems
- Analog IC design in Power Conversion




Inside a microchip – Silicon die

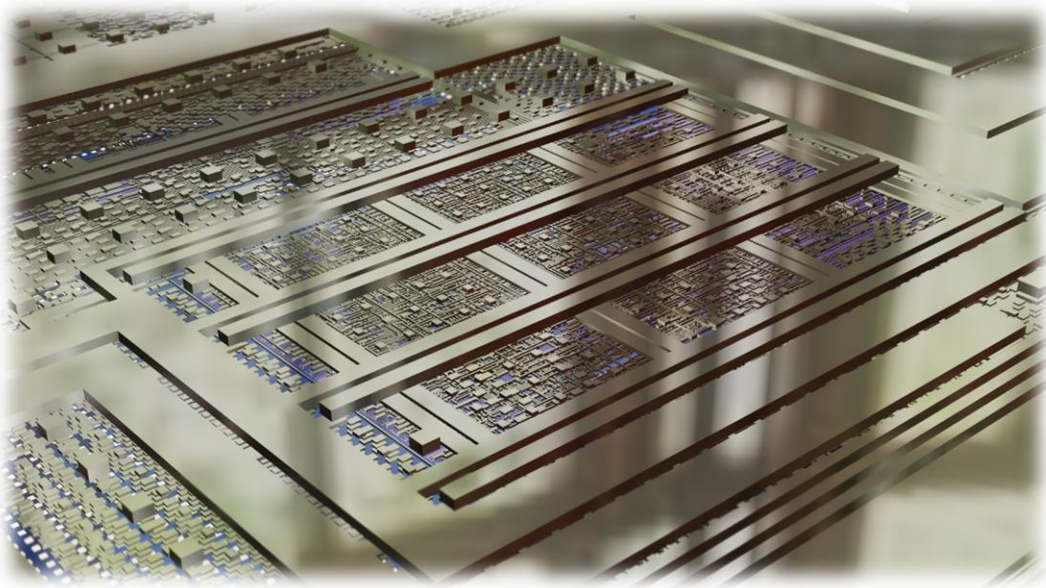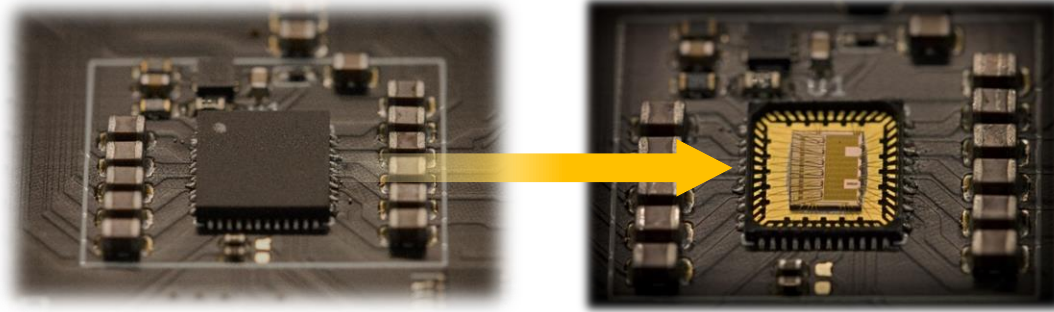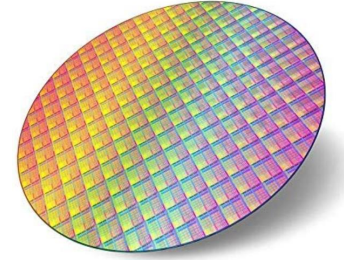

Implementation of Electronic Circuits

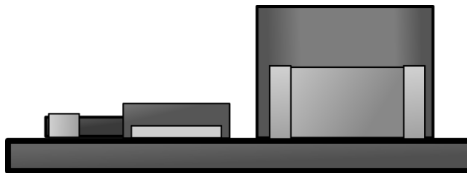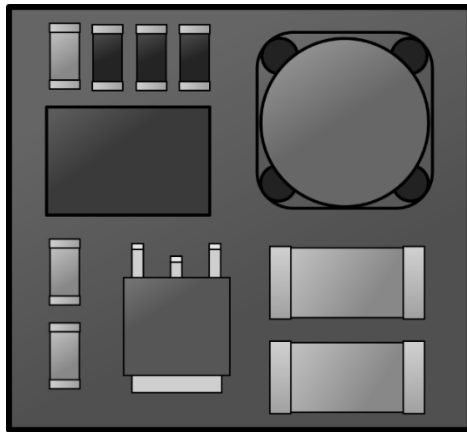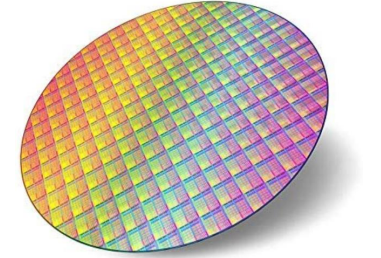


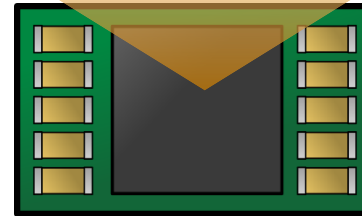Discrete component implementation
(Electronics Engineer)




Integrated circuits implementation
(Integrated Circuit Designer)

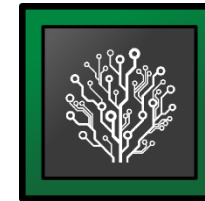Different design flow and tools, e.g., Cadence Virtuoso.




Advantages of IC design

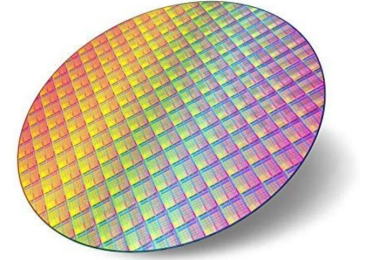

- Custom designed integrated circuits
- Custom functionalities and features
- Enables tradeoff optimization:
 - Performance vs power consumption
 - Size vs power consumption
- IC design makes certain systems possible
e.g. Microprocessors, hearing aids, extreme-power density power converters, etc.
- Chip art!


Wide range of applications

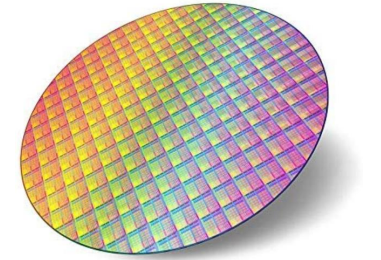



- Analog IC design covers a wide range of applications:
 - **Audio Systems**, e.g. Hearing aids, headphones, ...
 - **Power Conversion**, e.g. Power converters, gate drivers, ...
 - **High-speed communications**, e.g. Data centers, 5G transceivers, ...
 - **Sensors**, e.g. image sensors, temperature sensors, ...
 - ... and many more!

Agenda – Analog IC design

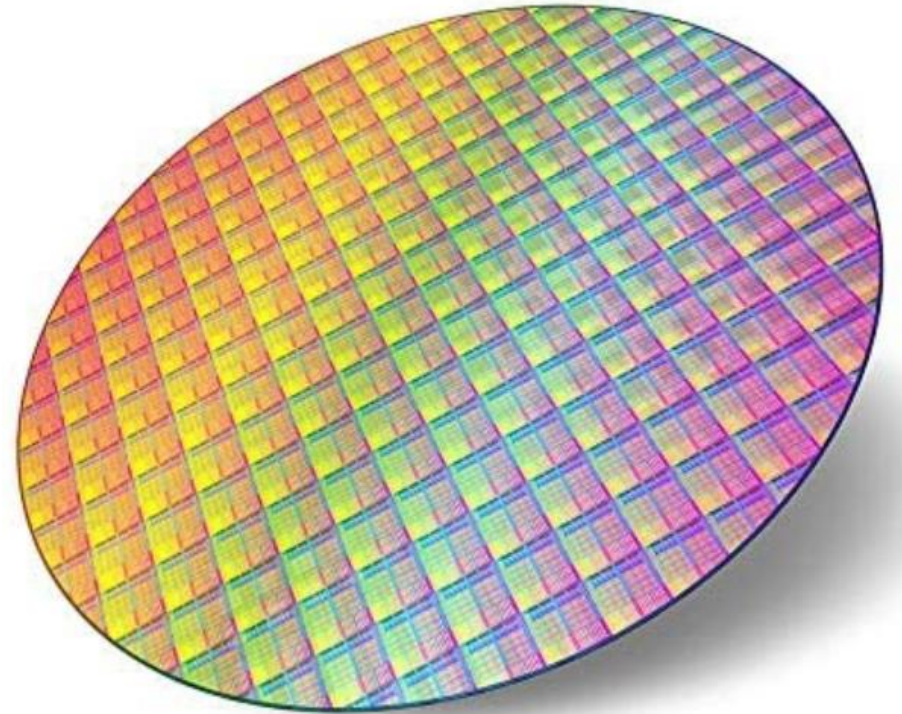- Background: What is Analog IC Design?
- Analog IC design in Audio Systems
- Analog IC design in Power Conversion




Audio input – block diagram

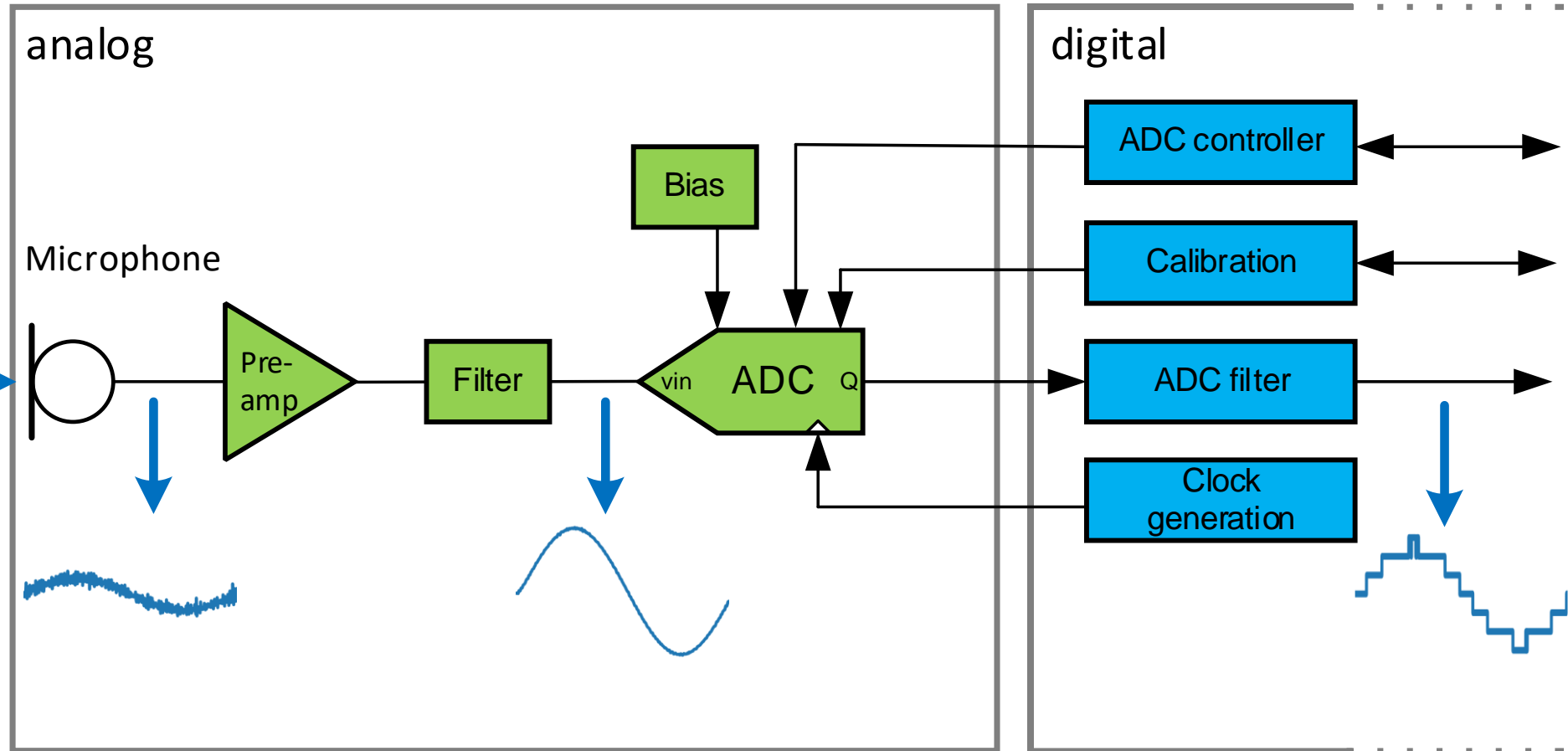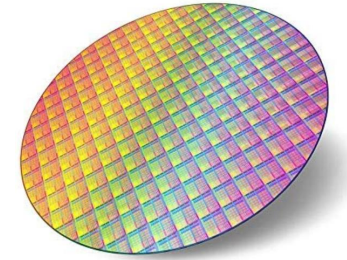


4-bit 

10-bit 



ADC example (sigma-delta)

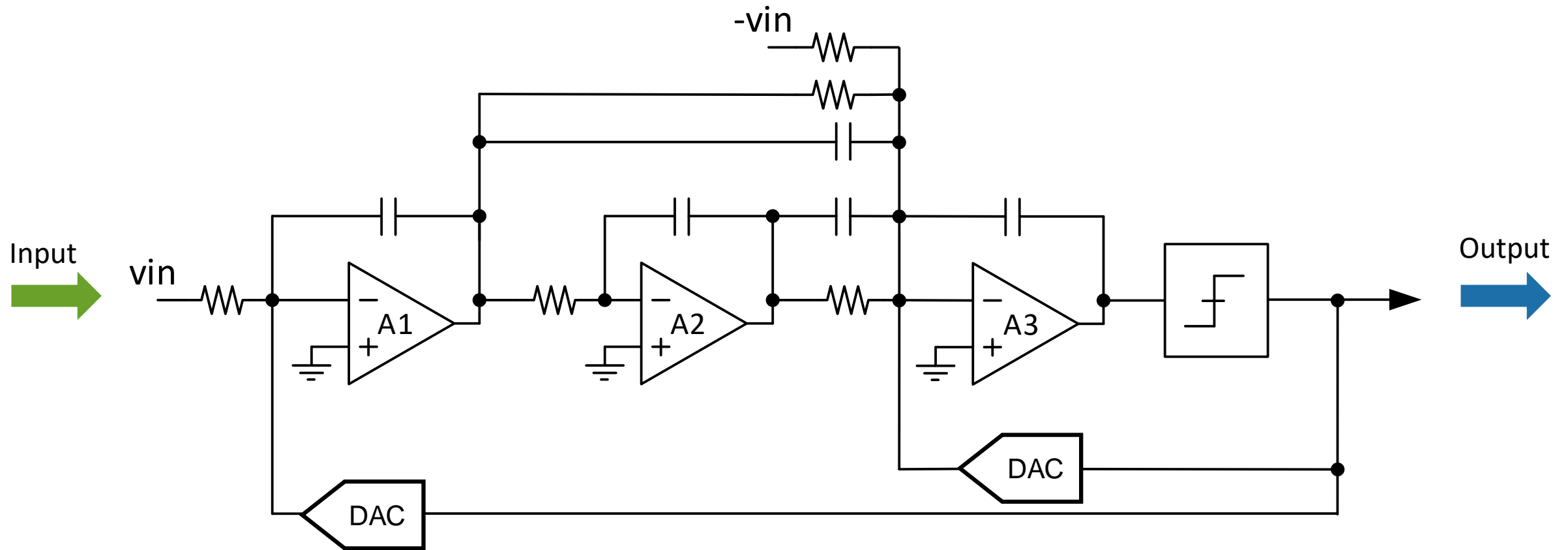

ADC example /






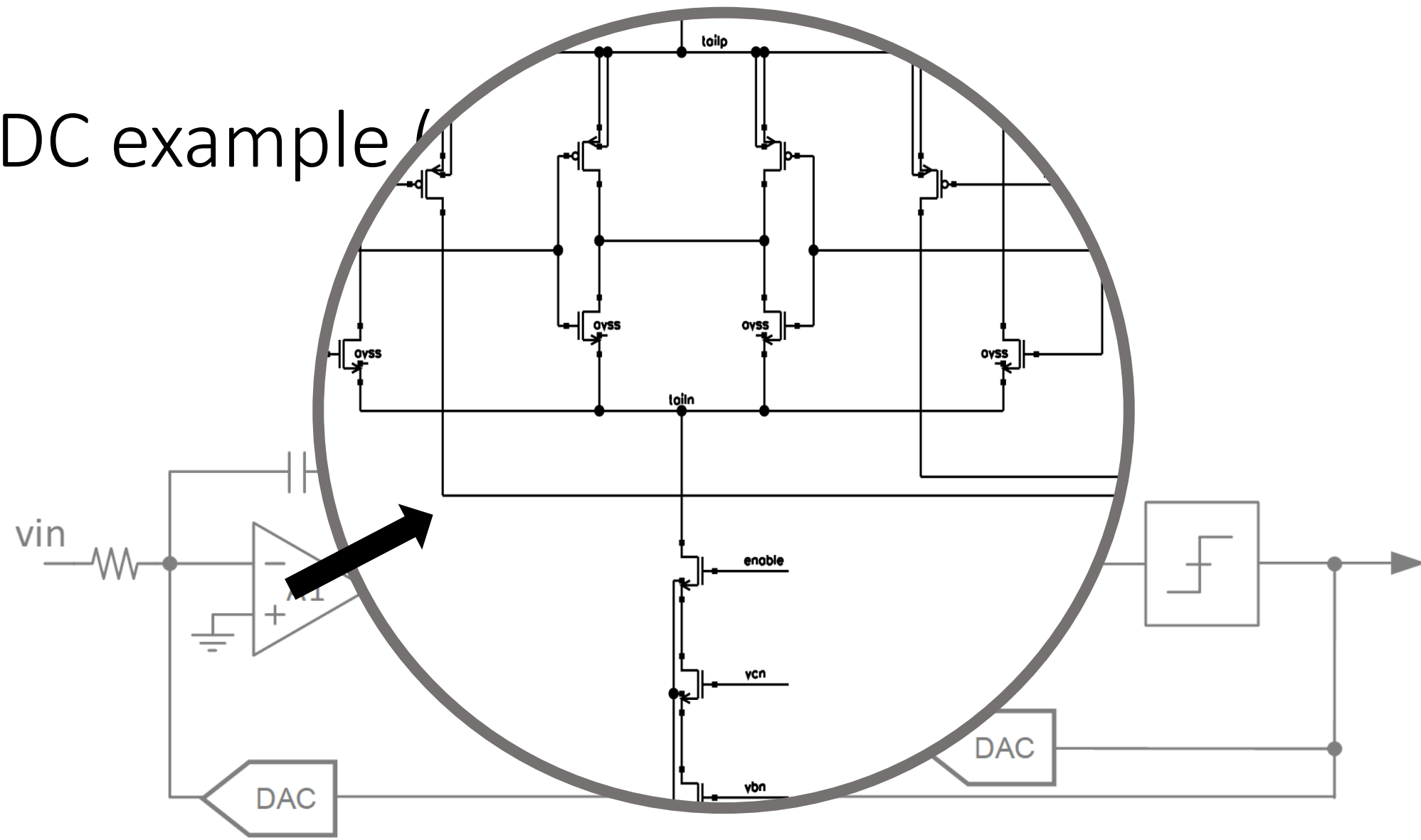


Audio input – layout view

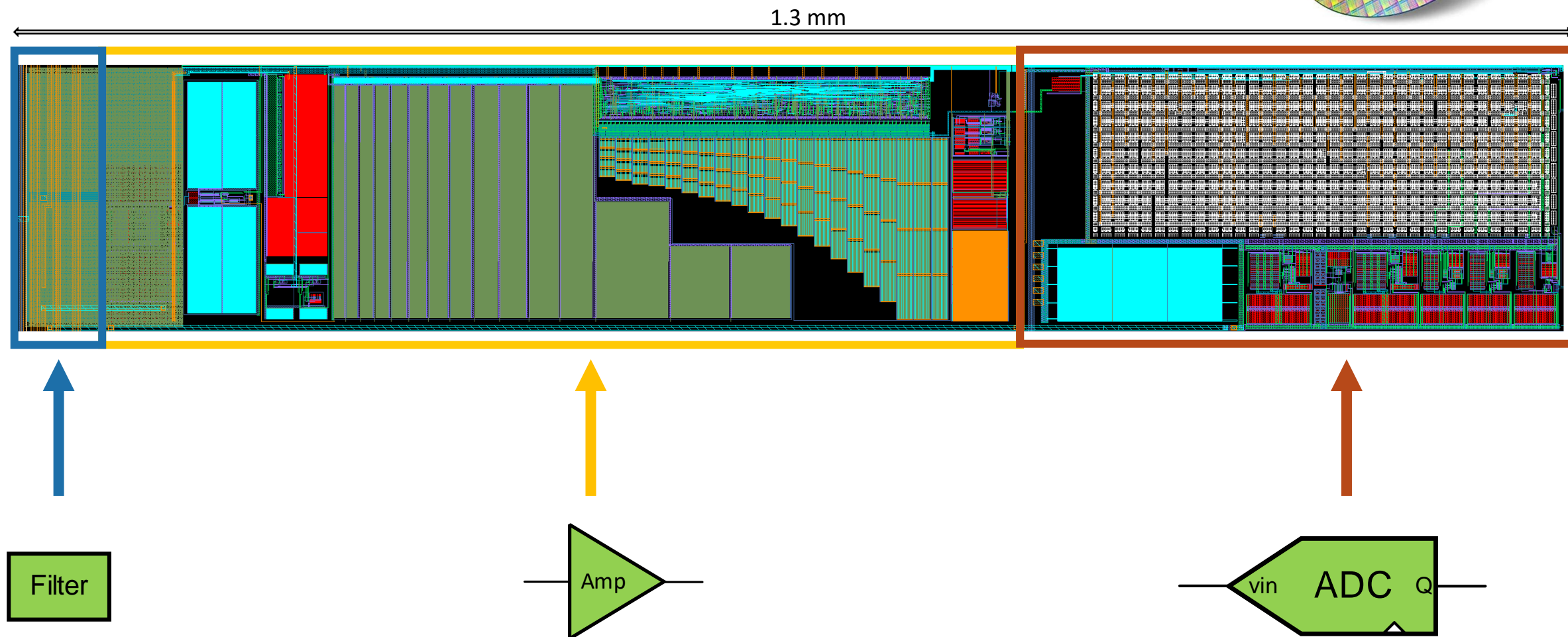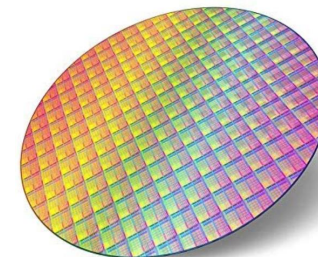


Audio input – layout view

Zoom in of the ADC

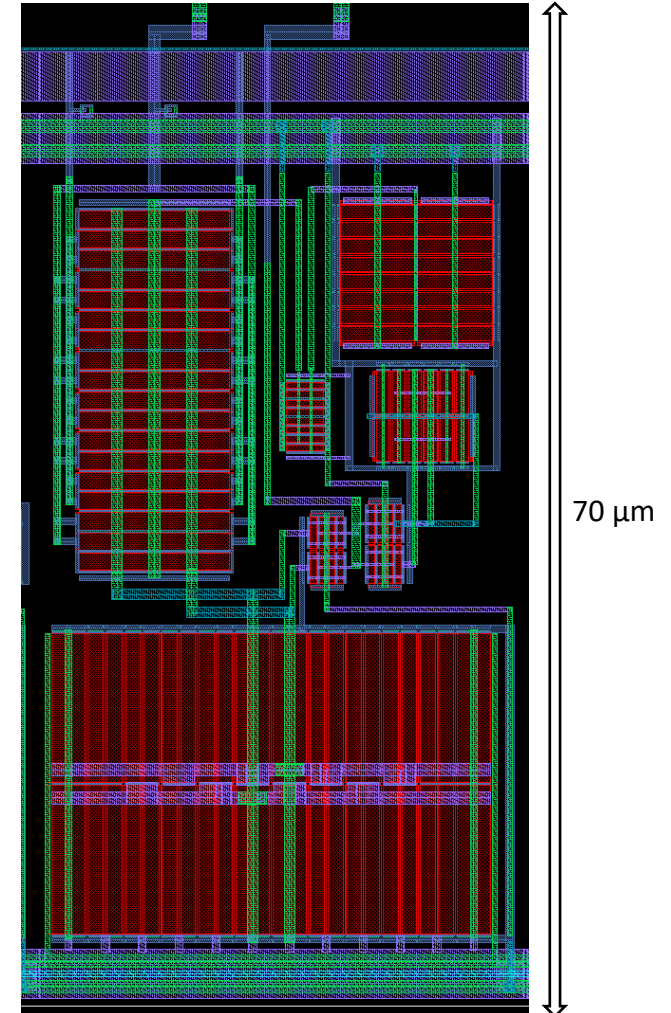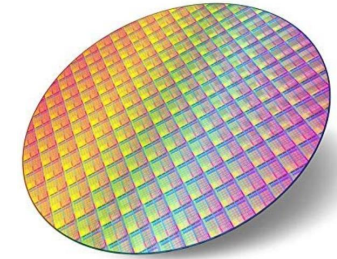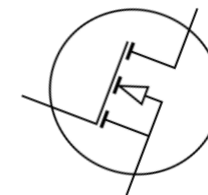 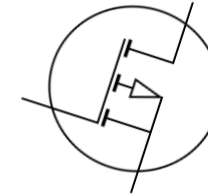
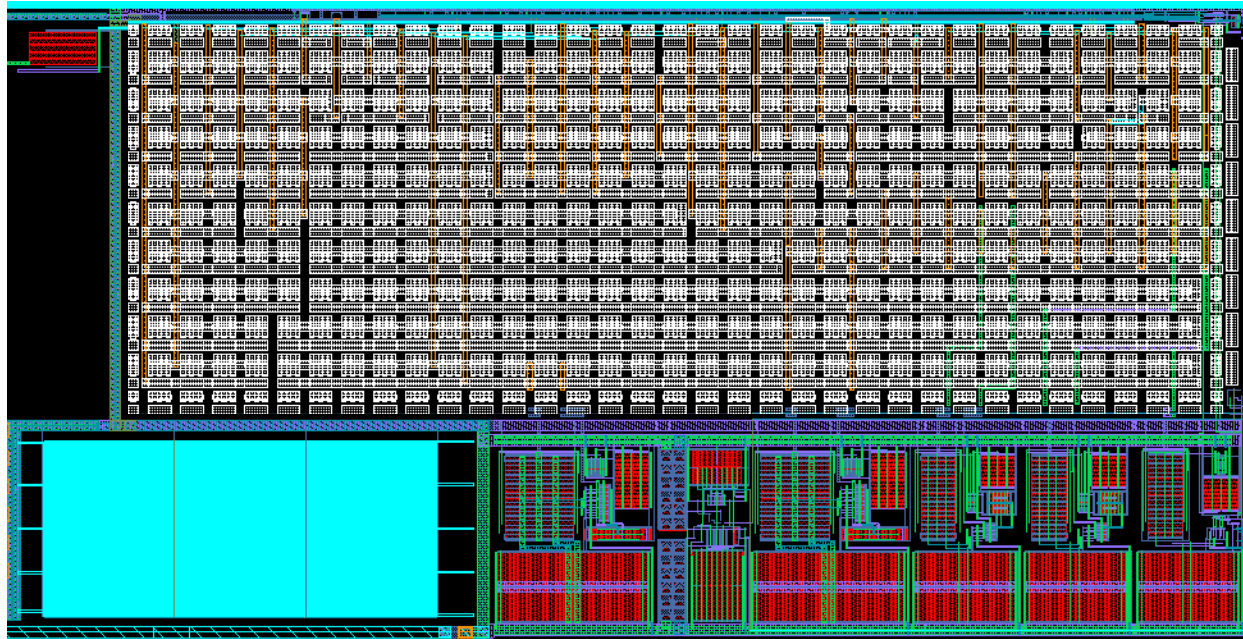


Agenda – Analog IC design

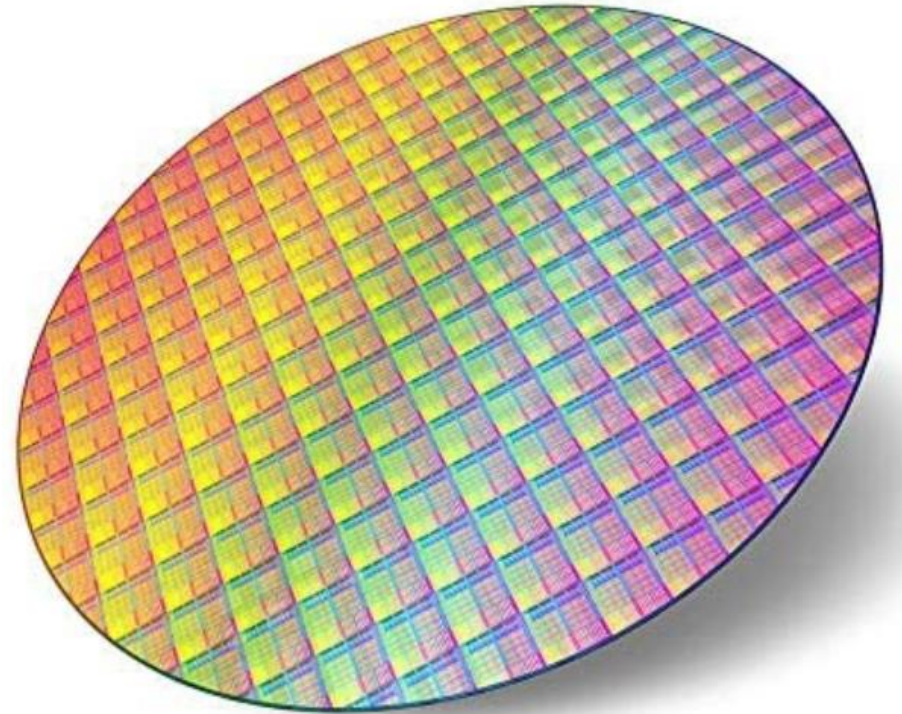- Background: What is Analog IC Design?
- Analog IC design in Audio Systems
- Analog IC design in Power Conversion



Power conversion basics

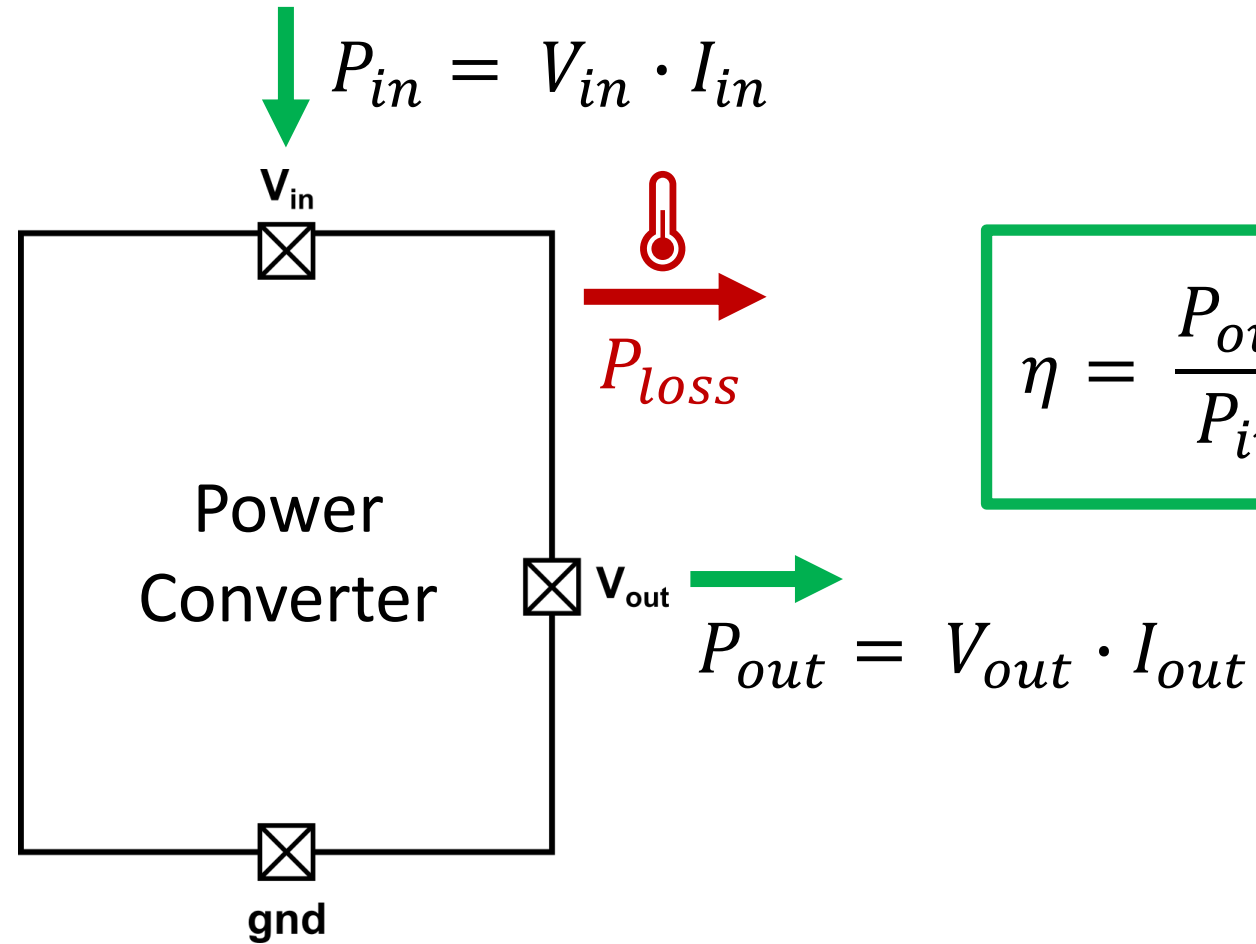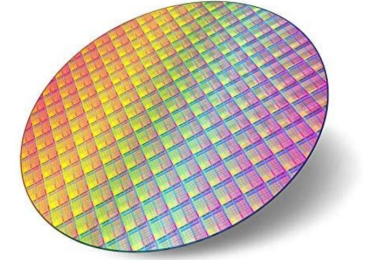


$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{in} - P_{loss}}{P_{in}}$$


Power conversion IC example

Switched-Capacitor Power Converter (SCPC)

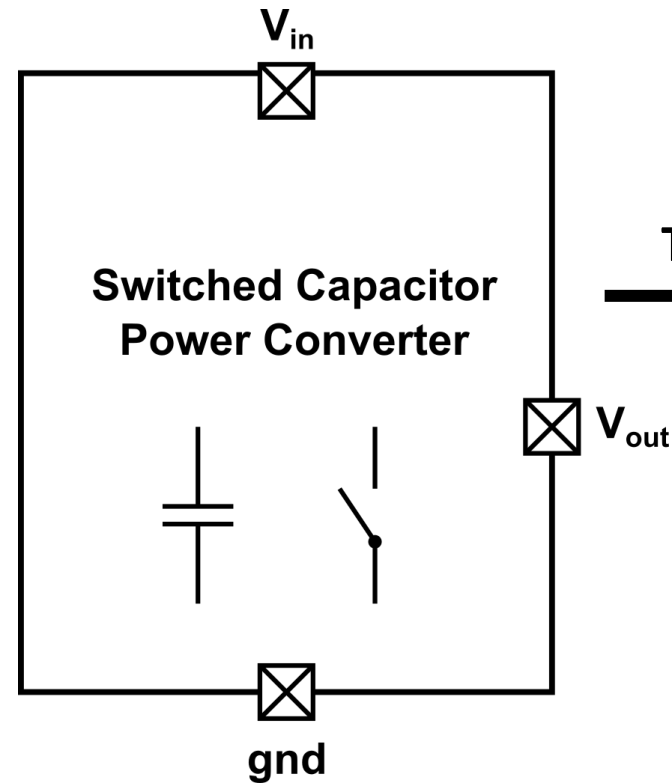
- $V_{in} = 48\text{ V}$
- $V_{out} = 12\text{ V}$
- $I_{out} = 1.6\text{ A}$




Topology

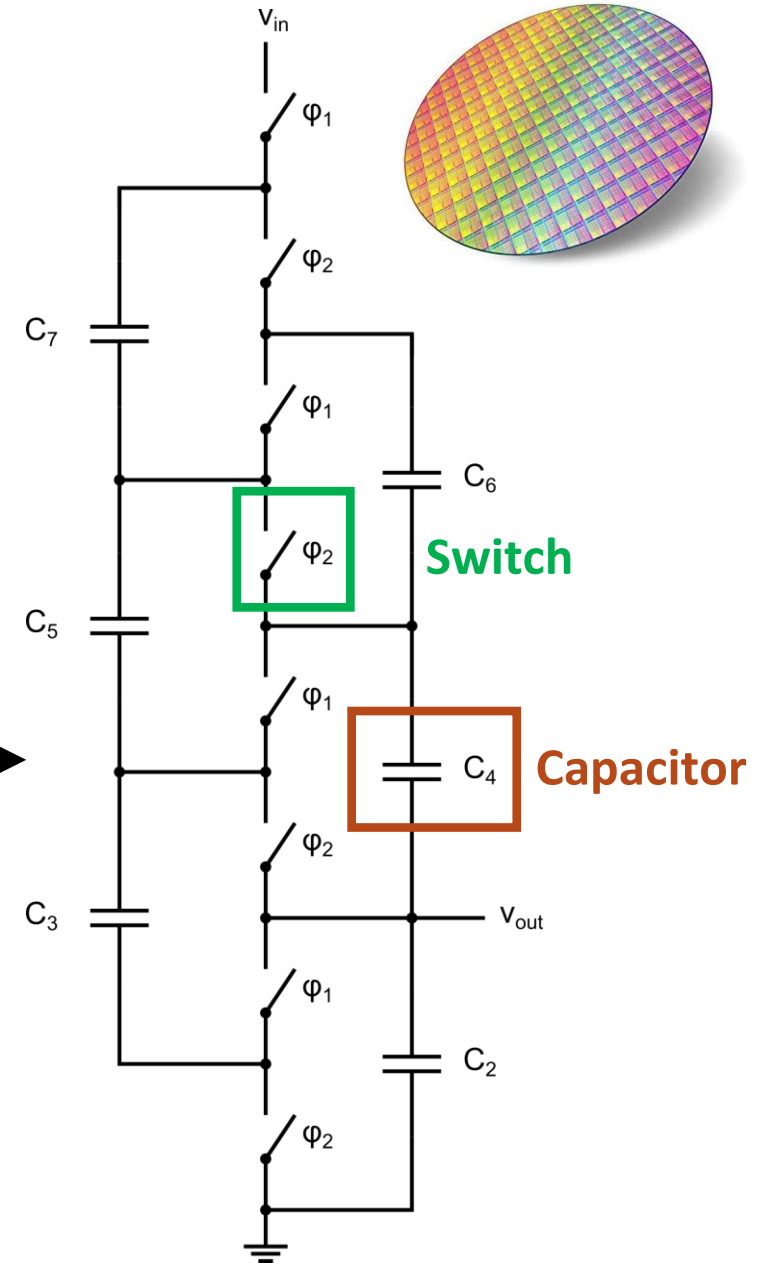


Switched-Capacitor Basic Components

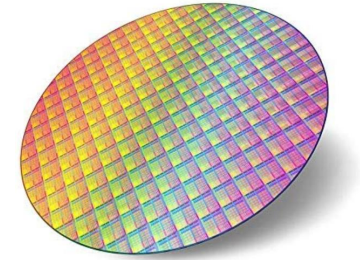

- Capacitors

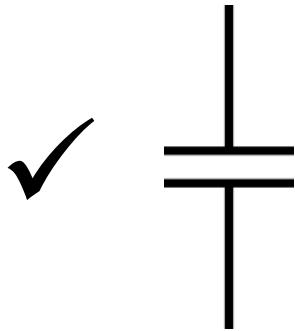

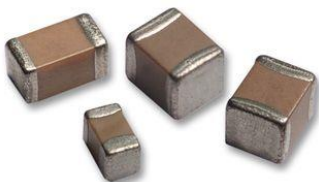- Discrete capacitors
- On-chip capacitors




- Switches



- Discrete switches
- Integrated switches



- Switch implementation

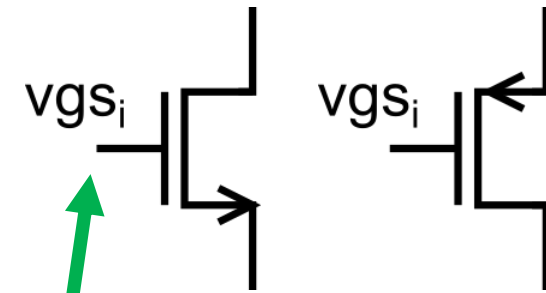



- Integrated NMOS
- Integrated PMOS
- ...

How do we drive them?


Gate driver and sub-circuits

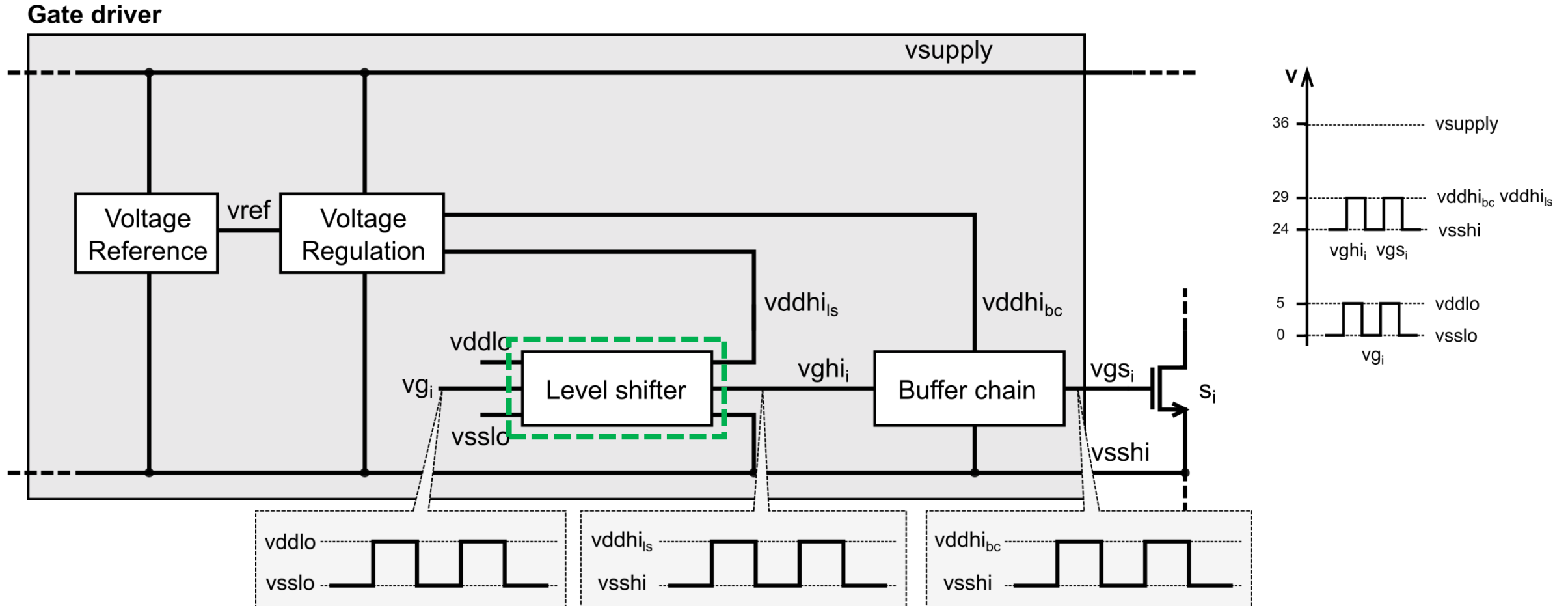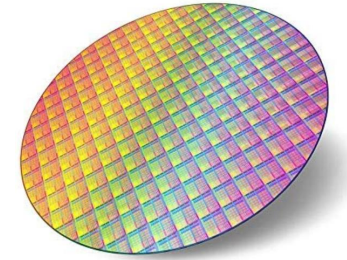

Subcircuit example: Level shifter



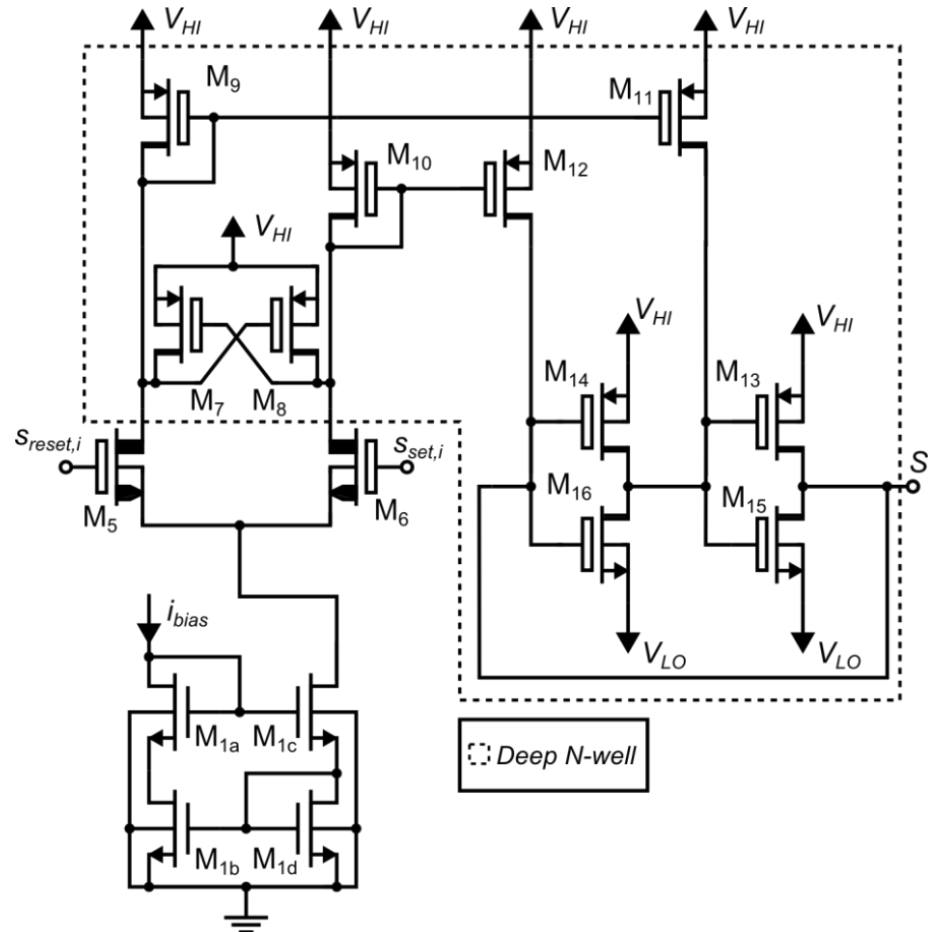
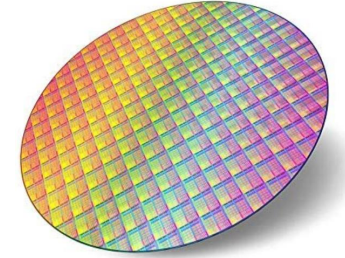


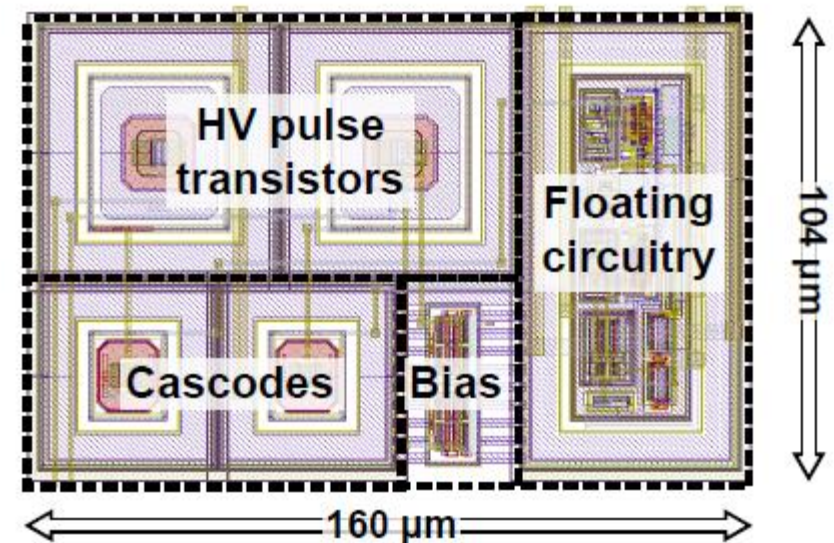- Pulse-triggered level shifter
- Transistor-level implementation schematic
- Different transistor types for different voltage levels
- Layout:







Gate driver within the IC

Gate driver

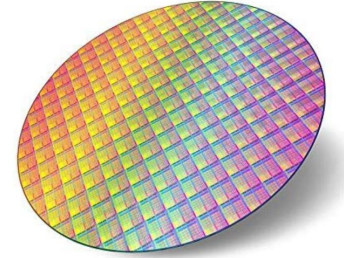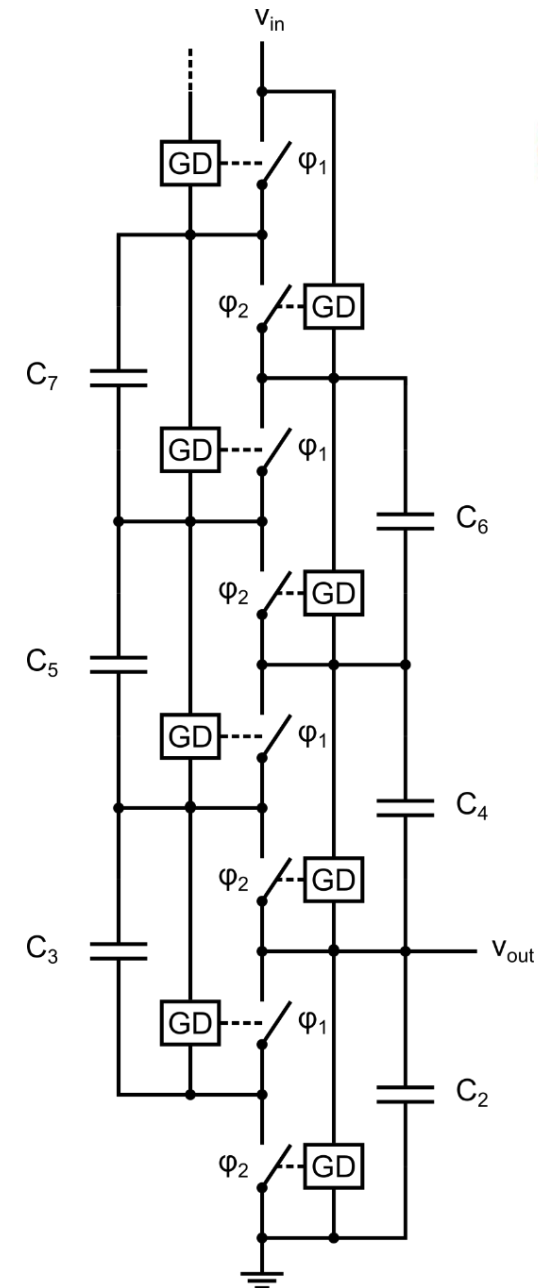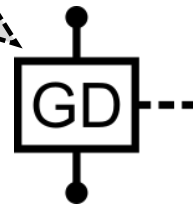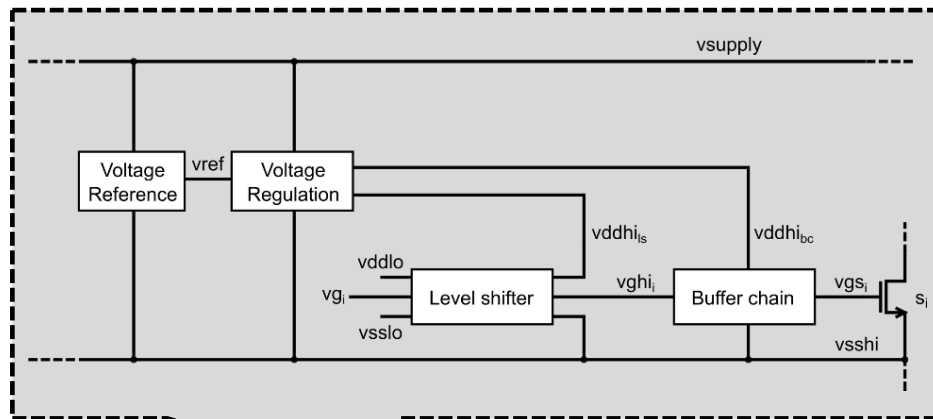

Overview of the IC (simplified)

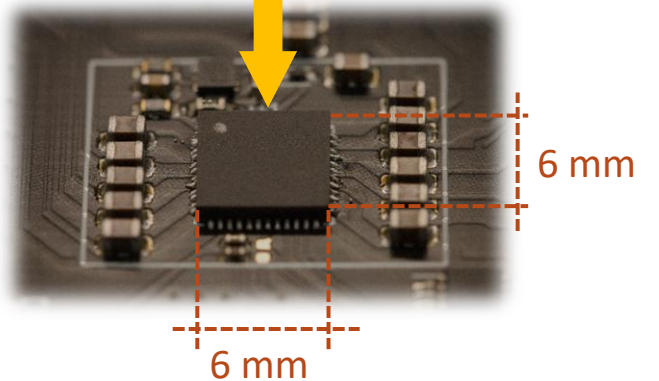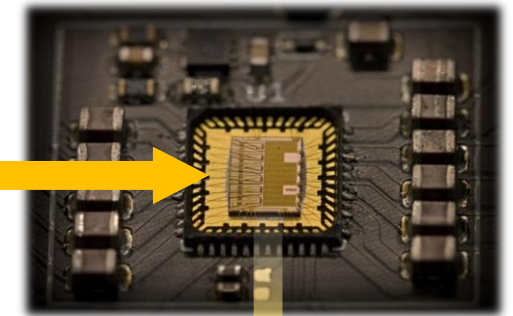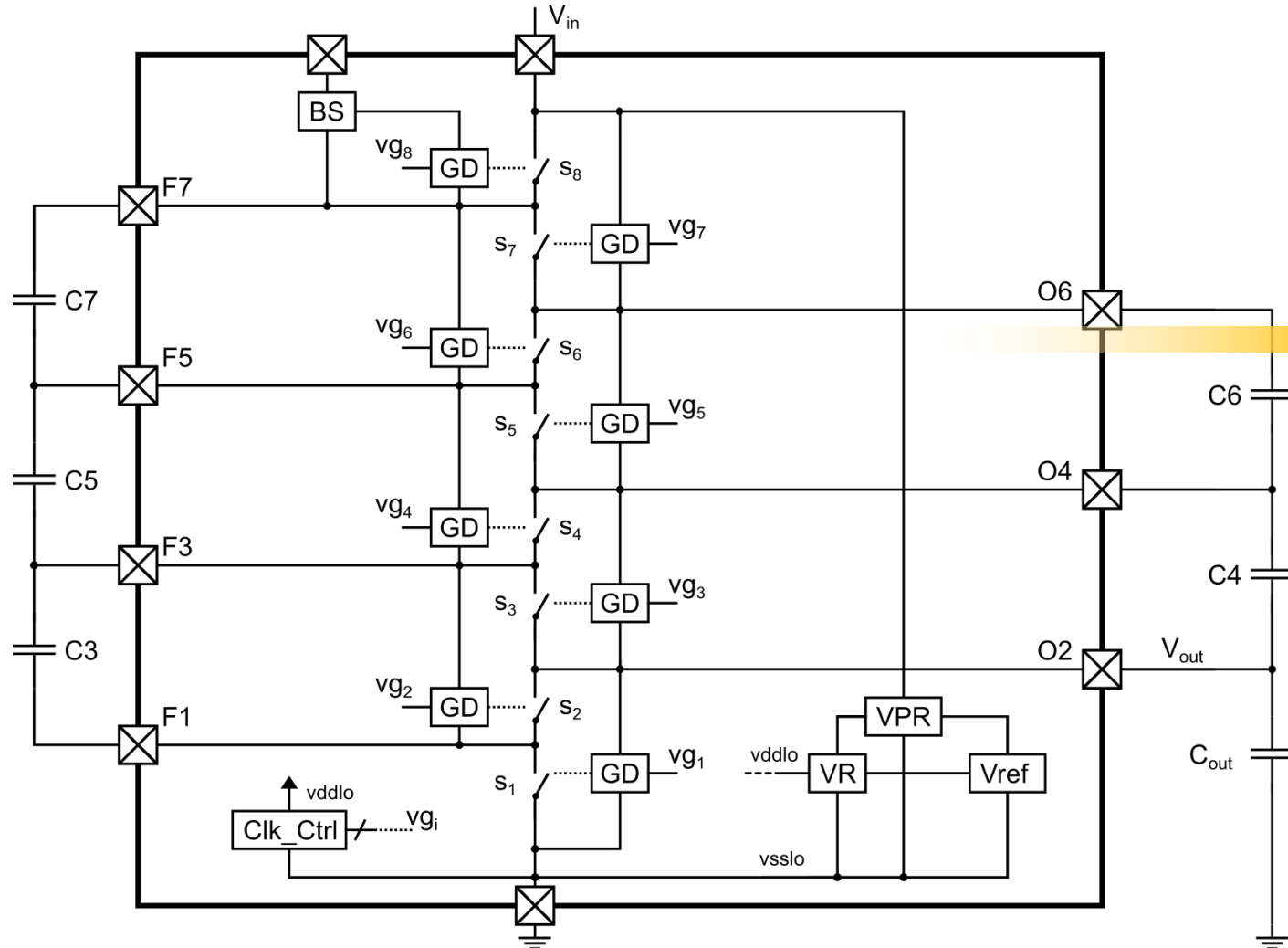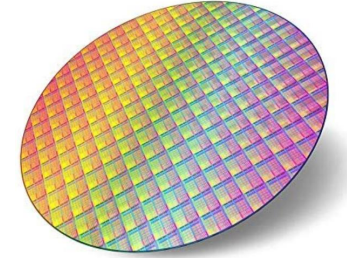

Thank You

