 


Digital Low-Power: World Domination

WS Audiology
Oticon



RTL - Register Transfer Logic


RTL written in Verilog or VHDL

```
always_ff @(posedge clk)
  in_reg <= in;


always_comb begin
  temp = in_reg[1] + in_reg[2];
  out_nxt = temp * in_reg[3];
end

always_ff @(posedge clk)
  out <= out_nxt;
```

Synthesis

 

Gates

 


Beware: synthesis allowed to mangle/restructure logic cloud. Often not important, but occasionally it is!

Let's Design

Higher level model or description e.g., Word, Matlab or Python:

```
>>> inp1 = 4
>>> inp2 = 9
>>> sum = inp1 + inp2
>>> print sum
13
>>> █
```

Mental picture:

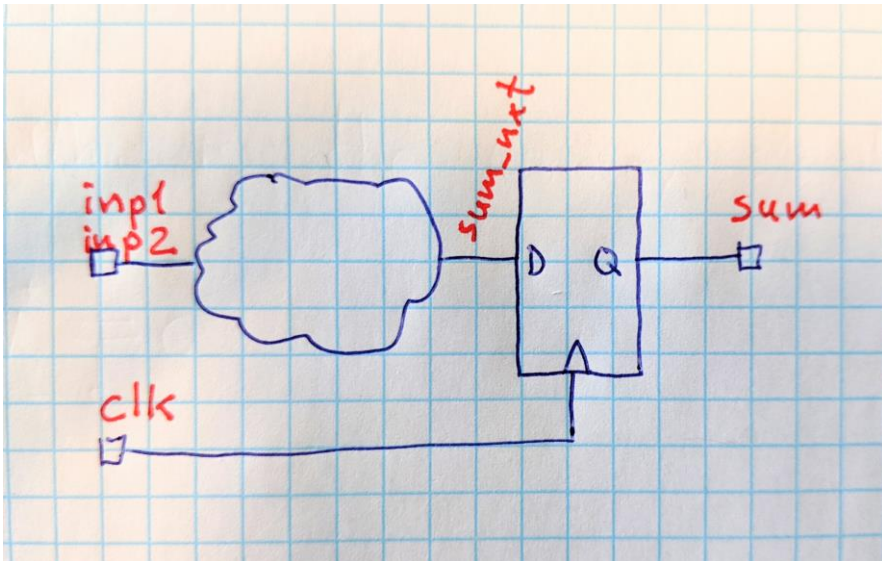

RTL:

```
module conquer_world (clk, inp1, inp2, sum);
    input clk;
    input [3:0] inp1, inp2;
    output logic [3:0] sum;


    logic [3:0] sum_nxt;
    always_comb
        sum_nxt = inp1 + inp2;

    always_ff @(posedge clk)
        sum <= sum_nxt;





endmodule
```

Synthesis - converting RTL to gates

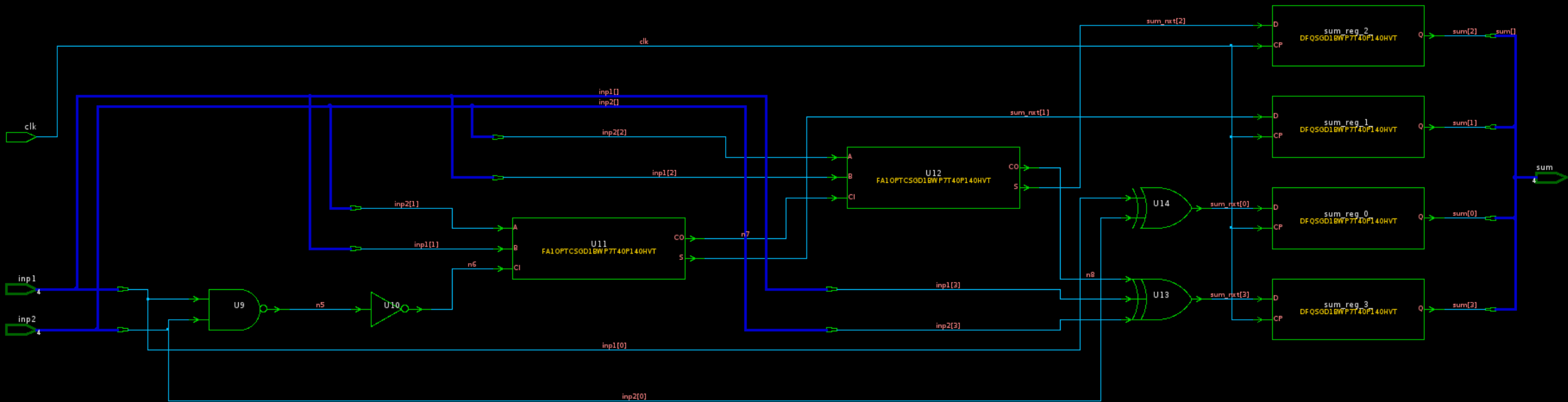
```
module conquer_world (clk, inp1, inp2, sum);  
    input clk;  
    input [3:0] inp1, inp2;  
    output logic [3:0] sum;  
  
    logic [3:0] sum_nxt;  
    always_comb  
        sum_nxt = inp1 + inp2;  
  
    always_ff @(posedge clk)  
        sum <= sum_nxt;  
  
endmodule
```



Place Route of Gates

   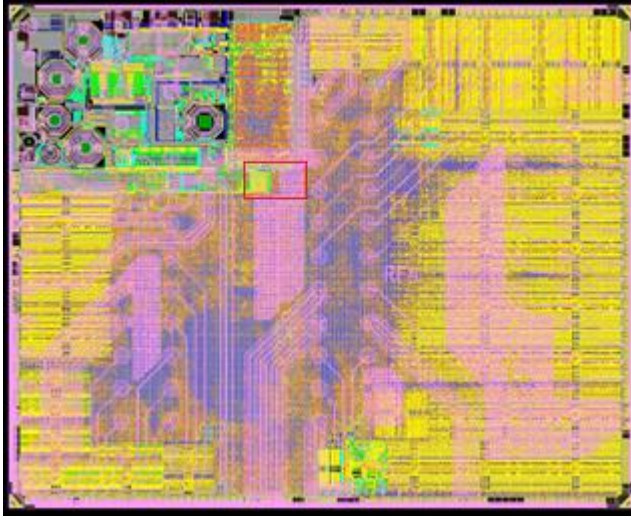


Low-Power Basics

 

$$E = \frac{1}{2} C V^2$$

Q: What is the energy on the capacitor ?
 
$$A: 1/2 * 20\text{fF} * (1\text{V})^2 = 10 \text{ fJ}$$


$$P = f \cdot E$$


$$P = f \cdot c \cdot v^2$$

Q: How much power does it use ?

A: $100 \text{ MHz} * 2 * 10 \text{ fJ} = 2 \text{ uW}$

Low-Power Design - Prevent Toggling

Mental model

 

Original RTL

```
module conquer_world (clk, inp1, inp2, sum);
    input clk;
    input [3:0] inp1, inp2;
    output logic [3:0] sum;

    logic [3:0] sum_nxt;
    always_comb
        sum_nxt = inp1 + inp2;

    always_ff @(posedge clk)
        sum <= sum_nxt;

endmodule
```

Low-Power RTL

```
module conquer_world (clk, en1, inp1, inp2, sum);
    input clk, en1;
    input [3:0] inp1, inp2;
    output logic [3:0] sum;

    logic [3:0] inp1a, inp2a;
    always_comb
        if (!en) begin
            inp1a = 0;
            inp2a = 0;
        end else begin
            inp1a = inp1;
            inp2a = inp2;
        end


    logic [3:0] sum_nxt;
    always_comb
        sum_nxt = inp1a + inp2a;

    always_ff @(posedge clk)
        sum <= sum_nxt;

endmodule
```

Low-Power Design - Prevent Toggling

```
module conquer_world (clk, en1, inp1, inp2, sum);  
    input clk, en1;  
    input [3:0] inp1, inp2;  
    output logic [3:0] sum;  
  
    logic [3:0] inp1a, inp2a;  
    always_comb  
        if (!en) begin  
            inp1a = 0;  
            inp2a = 0;  
        end else begin  
            inp1a = inp1;  
            inp2a = inp2;  
        end  
  
    logic [3:0] sum_next;  
    always_comb  
        sum_next = inp1a + inp2a;  
  
    always_ff @(posedge clk)  
        sum <= sum_next;  
endmodule
```

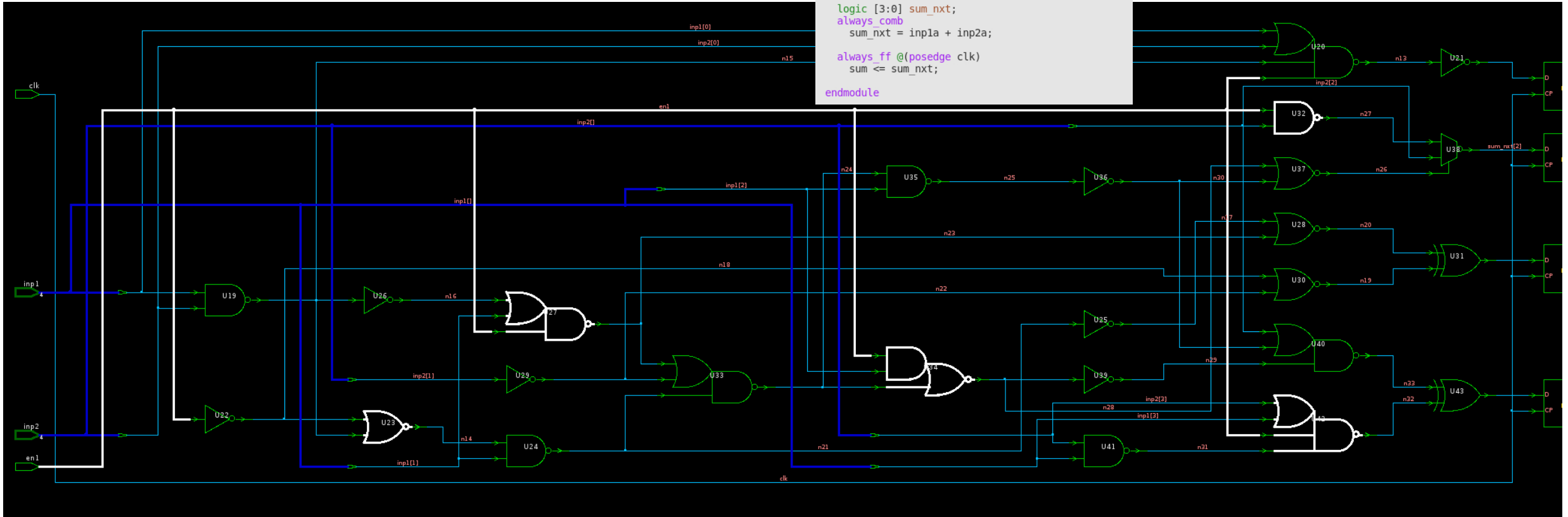

Junior Digital Designer: WTF. This is not what I wrote in RTL !

Senior Digital Designer: You forgot the slide at the beginning: synthesis allowed to restructure expression, keeping final expression intact

Low-Power Design - Clock Gating

Flop clock input: $0.4 \text{ uW}/\text{clk_input}$ (100MHz)

Clock-gater input: 0.1 uW (100MHz)

Q: how much power did the clock-gater save (assume mostly stopping the clock) ?

A: before $4 \times 0.4 \text{ uW}$, after 0.1 uW , saved 1.5 uW

```
module conquer_world (clk, inp1, inp2, sum);
  input clk;
  input [3:0] inp1, inp2;
  output logic [3:0] sum;




  logic [3:0] sum_nxt;
  always_comb
    sum_nxt = inp1 + inp2;

  always_ff @(posedge clk)
    sum <= sum_nxt;
endmodule
```

```
module conquer_world (clk, en1, inp1, inp2, sum);
  input clk, en1;
  input [3:0] inp1, inp2;
  output logic [3:0] sum;

  logic [3:0] sum_nxt;
  always_comb
    sum_nxt = inp1 + inp2;

     always_ff @(posedge clk)
    if (en1)
      sum <= sum_nxt;
endmodule
```



Low-Power Design - Clock Gating

```


module conquer_world (clk, en1, inp1, inp2, sum);
  input clk, en1;
  input [3:0] inp1, inp2;
  output logic [3:0] sum;

  logic [3:0] sum_nxt;
  always comb
    sum_nxt = inp1 + inp2;

  always ff @(posedge clk)
    if (en1)
      sum <= sum_nxt;

endmodule

```

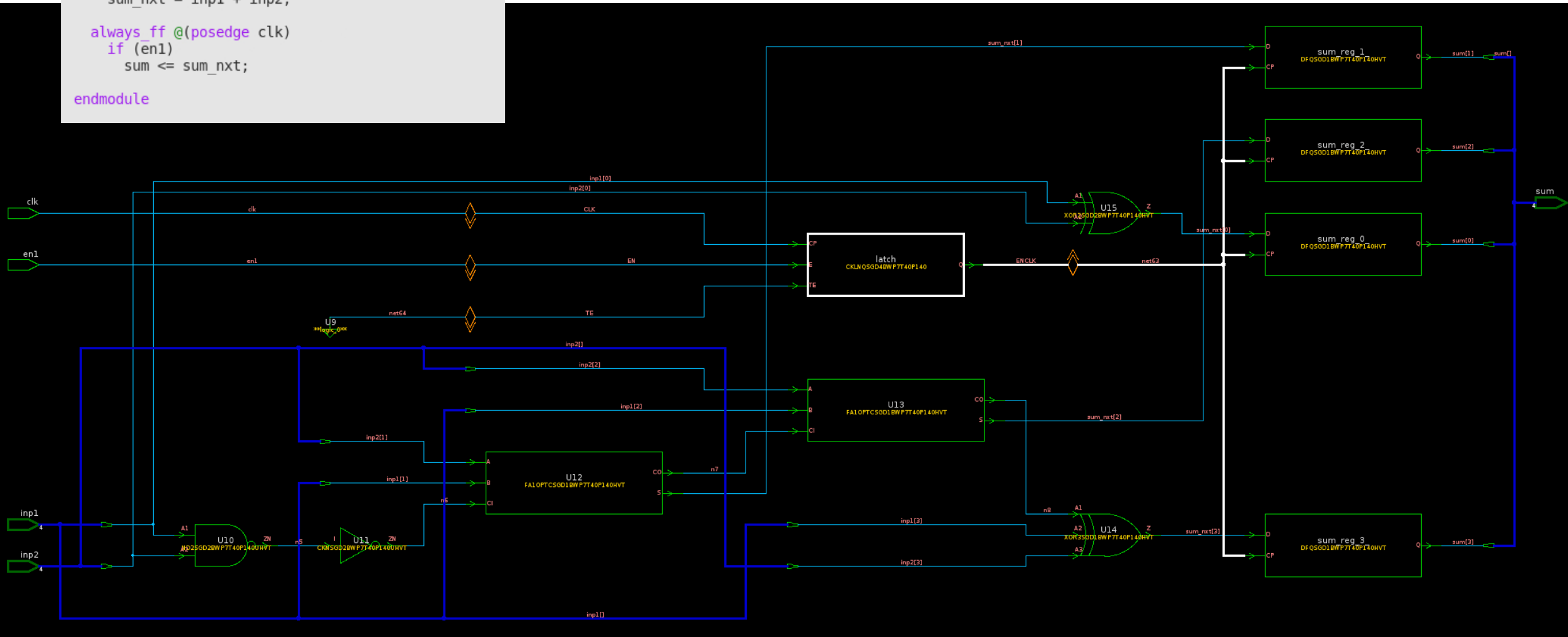

Ready to take over the world ?

